

College of Electronic Technology– Tripoli

Final-exam -Term: Spring 2020

Department: Communication Engineering

Subject: Dynamic Systems & Control

Semester: 5<sup>th</sup>

Examiner: Dr. Mosa Abdesalam


Marks: 40.

Allowed Time: 2.00 hrs.

### Problem 1: Transfer Function for RLC (10 points)


The network shown in Figure below. Assume that  $v_i(t)$  is the input and  $v_o(t)$  is the output. The output is the voltage through  $L_2$  as shown in the figure as  $(+ V_L(t) -)$ .

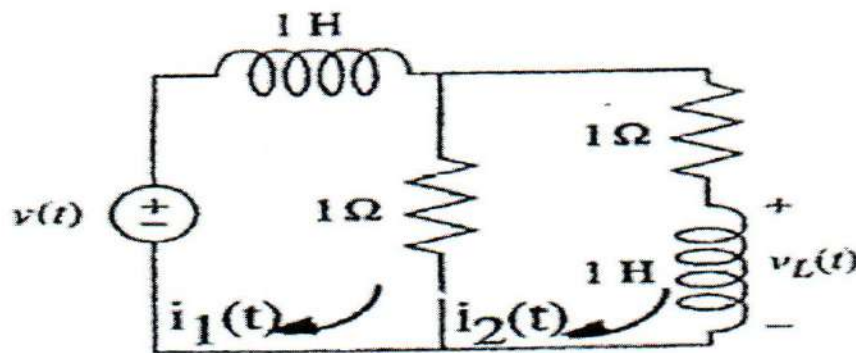1. Find the transfer function representation. (5 points)
2. Find the inverse Laplace transform of the  $v_o(t)$ . First, perform the partial fraction expansion on  $v_o(s)$ , where the input is unit step response ( $v_i(s) = \frac{1}{s}$ ). (5 points)


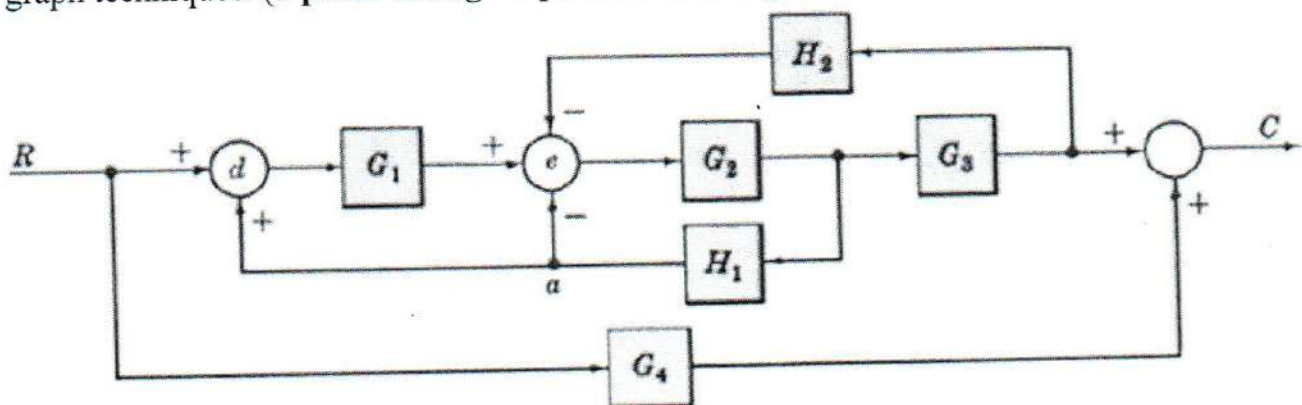
### Problem 2: signal flow graph. (10 points)

Determine the transfer function  $(C(s)/R(s))$  for the block diagram below by signal flow graph techniques. (3 point-chang +7 point Mason's gain formula)



### Problem 3: First Order Systems. (10 points)

Find the transfer function,  $V_o(s)/V_i(s)$ , for the circuit in Figure below. Where  $R = 1 \Omega$ , and  $L = 1H$ .

Do the following:

1. Determine the transfer function  $\frac{C(s)}{R(s)} = V_o(s)/V_i(s)$ .
2. Draw the step response of the network. Where the input is unit step response ( $R(s) = \frac{1}{s}$ ).
3. Determine the values of time constant, rise time, settling time, and steady state error.
4. For the system shown figure below evaluate the static error constants  $K_p$ ,  $K_v$  and  $K_a$  and find the expected steady state errors for the unit step, ramp and parabolic inputs.


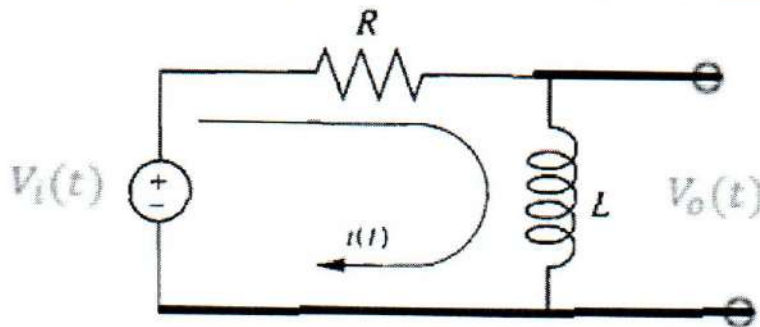


FIGURE *RL* network

### Problem 4: Second Order Systems. (10 points)

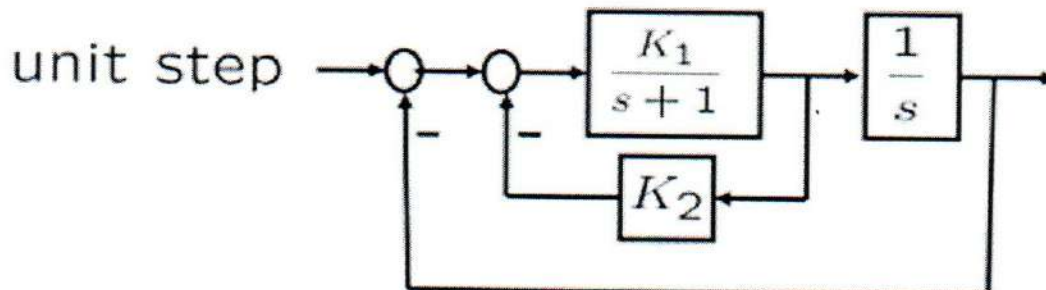1. For the system shown in Figure below, determine the values of gain  $K_1$  and  $K_2$  so that the maximum overshoot in the unit-step response is 0.163 and the peak time is 2 sec. With these values of  $K_1$  and  $K_2$ , obtain the rise time, settling time 2%, 5%,  $\beta$  and  $w_d$ .
2. Determine the static error constants  $K_p$ ,  $K_v$  and  $K_a$  and find the expected steady state errors for the unit step, ramp and parabolic inputs.



Good Luck.