

Q1)- {15 Marks}

a)- Given $\omega = 314 \text{ rad/s}$, determine how long it will take the sinusoidal waveform to pass through an angle of 90°

{7Marks}

b)- The current through a 0.2-H coil is provided. Find the sinusoidal expression for the voltage across the coil.
Sketch the v and i curves

{8Marks}



$$i(t) = 7 \sin(377t - 70^\circ)$$

Q2)-

{15 Marks}

The phasor diagram of Series RLC circuit is shown in the fig:

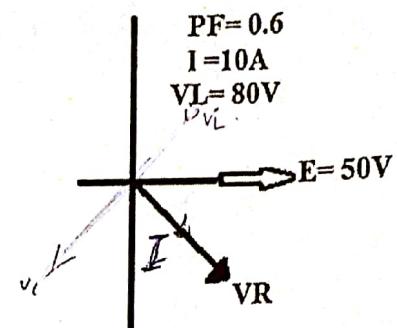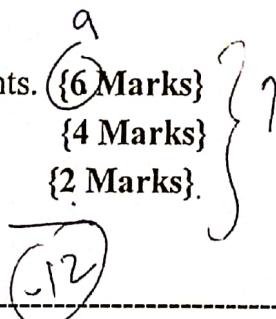- 1- Find The value of the series elements. {6 Marks}
- 2- Complete the phasor diagram . {4 Marks}
- 3- Determine P_{av} {2 Marks}



Q3)-


{15 Marks}

In the circuit shown,given that:

$$Z_1 = 3 - J4, \quad Z_2 = 4.426 + J4.426, \text{ and}$$

$$Z_3 = 2 - J3$$

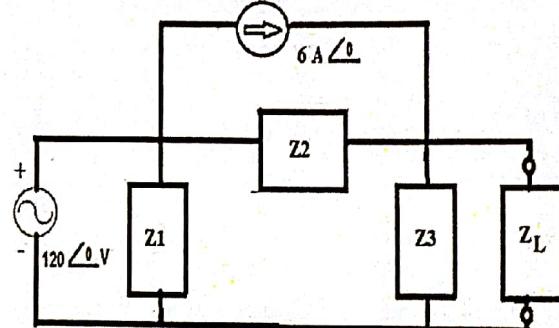- a)- Determine the value of Z_L for maximum power to the load. {6 Marks}
- b)-Find P_{max} {9 Marks}



Q4)-

{15 Marks}

For the System shown:

- a)- Draw the power triangle. {9 Marks}
- b)- Find total power factor. {3 Marks}
- c)- Determine the total current I_T . {3 Marks}

